

*ELEC0014 - Introduction to electric power and energy systems*

## The power transformer

Thierry Van Cutsem

`t.vancutsem@ulg.ac.be`

`www.montefiore.ulg.ac.be/~vct`


November 2019

Power transformers are used:

- to transmit electrical energy under high voltages
  - step-up transformers at the terminal of generators
  - step-down transformers to distribute energy at the end-users
- to control the voltages at some busbars:
  - in sub-transmission networks
  - in distribution networks
- to control the power flows in some parts of a meshed network.

# The single-phase transformer

## Principle

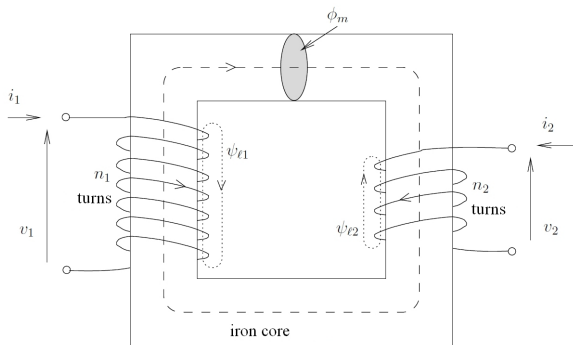

step-up transformer: secondary voltage  $>$  primary voltage

step-down transformer: secondary voltage  $<$  primary voltage.

alternating voltage  $v_1$  at terminals of coil 1  $\rightarrow$  alternating current  $i_1$  in coil 1  
 $\rightarrow$  alternating magnetic field  $\rightarrow$  voltage induced in coil 2  $\rightarrow$  current  $i_2$  in coil 2  
 $\rightarrow$  magnetic field superposed to the one created by  $i_1$ .

## Fluxes in coils

$$n_1 i_1 + n_2 i_2 = \mathcal{R} \phi_m$$

$\phi_m$  : magnetic flux in a cross section of the iron core

$\mathcal{R}$  : *reluctance* of the magnetic circuit

+ sign: due to the way coils are wound and the direction of currents

$$\psi_1 = \psi_{\ell 1} + n_1 \phi_m$$

$\psi_1$  : flux linkage in coil 1

$\psi_{\ell 1}$  : *leakage flux* in coil 1 (lines of magnetic field crossing coil 1 but not passing through the iron core)

$$\psi_2 = \psi_{\ell 2} + n_2 \phi_m$$

$\psi_2$  : flux linkage in coil 2


$\psi_{\ell 2}$  : *leakage flux* in coil 2 (lines of magnetic field crossing coil 2 but not passing through the iron core)

## Ideal transformer

- The coils have no resistance
- the coils have no leakage flux
- the permeability of the core material is infinite.

$$\mathcal{R} \simeq 0 \quad \Rightarrow \quad i_2 = -\frac{n_1}{n_2} i_1$$
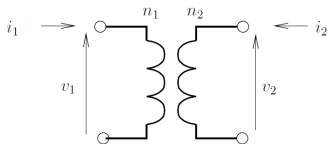
$$v_1 = \frac{d\psi_1}{dt} = n_1 \frac{d\phi_m}{dt} \quad v_2 = \frac{d\psi_2}{dt} = n_2 \frac{d\phi_m}{dt} \quad \Rightarrow \quad v_2 = \frac{n_2}{n_1} v_1$$



Step-down transformer:  $v_2 < v_1 \Rightarrow n_2 < n_1 \Rightarrow i_2 > i_1$   
 coil 2 has fewer turns but higher cross-sectional area

$$v_1 i_1 = -v_2 i_2 : \quad \text{no losses in the ideal transformer!}$$

## Equations of the real transformer

$$\text{Leakage inductances:} \quad L_{\ell 1} = \frac{\psi_{\ell 1}}{i_1} \quad L_{\ell 2} = \frac{\psi_{\ell 2}}{i_2}$$

$$\text{Magnetizing inductance (seen from coil 1):} \quad L_{m1} = \frac{n_1^2}{\mathcal{R}}$$

Flux linkages:

$$\psi_1 = L_{\ell 1} i_1 + n_1 \frac{n_1 i_1 + n_2 i_2}{\mathcal{R}} = L_{\ell 1} i_1 + \frac{n_1^2}{\mathcal{R}} i_1 + \frac{n_1 n_2}{\mathcal{R}} i_2 = L_{\ell 1} i_1 + L_{m1} i_1 + \frac{n_2}{n_1} L_{m1} i_2$$


$$\psi_2 = L_{\ell 2} i_2 + n_2 \frac{n_1 i_1 + n_2 i_2}{\mathcal{R}} = L_{\ell 2} i_2 + \frac{n_2^2}{\mathcal{R}} i_2 + \frac{n_1 n_2}{\mathcal{R}} i_1 = L_{\ell 2} i_2 + \left(\frac{n_2}{n_1}\right)^2 L_{m1} i_2 + \frac{n_2}{n_1} L_{m1} i_1$$

Voltages at the terminals of the coils:

$$v_1 = R_1 i_1 + \frac{d\psi_1}{dt} = R_1 i_1 + L_{\ell 1} \frac{di_1}{dt} + L_{m1} \frac{di_1}{dt} + \frac{n_2}{n_1} L_{m1} \frac{di_2}{dt}$$

$$v_2 = R_2 i_2 + \frac{d\psi_2}{dt} = R_2 i_2 + L_{\ell 2} \frac{di_2}{dt} + \left(\frac{n_2}{n_1}\right)^2 L_{m1} \frac{di_2}{dt} + \frac{n_2}{n_1} L_{m1} \frac{di_1}{dt}$$

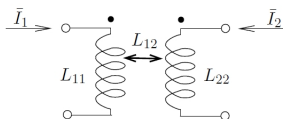The transformer is a particular case of magnetically coupled circuits




- if the currents enter by the terminals marked with  $\bullet$ , their contributions to the flux  $\phi_m$  are added
- if the currents are counted positive when entering the terminals marked with  $\bullet$ , the mutual inductance is positive
- the  $\bullet$  also indicate AC voltages which are in phase when the transformer is supposed ideal.

One easily identifies:


$$L_{11} = L_{\ell 1} + \frac{n_1^2}{\mathcal{R}} \quad L_{12} = \frac{n_1 n_2}{\mathcal{R}} \quad L_{22} = L_{\ell 2} + \frac{n_2^2}{\mathcal{R}}$$
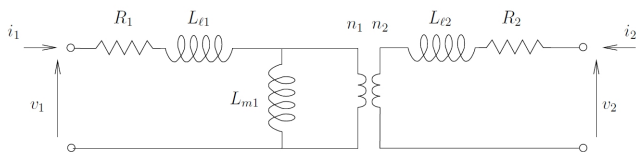
## Equivalent circuits of the real transformer



$$R_1 i_1^2 + R_2 i_2^2 : \text{copper losses}$$

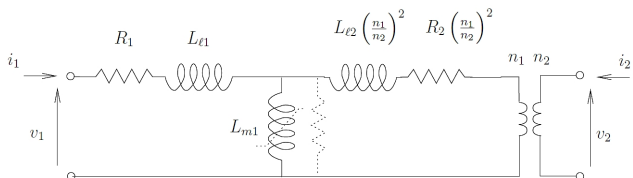Passing  $R_2$  et  $L_{\ell 2}$  from side 2 to side 1:



Possible improvements:


- shunt resistance to account for *iron losses* (due to eddy currents)
  - kept small by using laminated cores
  - negligible compared to the power passing through the transformer
- non-linear inductance  $L_{m1}$  to account for iron saturation.


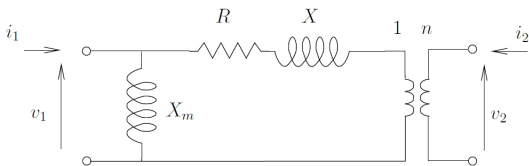
## Usual simplified equivalent circuit

Usual simplification taking into account that:

$$\omega L_{m1} \gg R_1, R_2, \omega L_{\ell 1}, \omega L_{\ell 2}$$




$$n = \frac{n_2}{n_1} \quad R = R_1 + \frac{R_2}{n^2} \quad X = \omega L_{\ell 1} + \frac{\omega L_{\ell 2}}{n^2} \quad X_m = \omega L_{m1}$$

- Equivalent circuit justified by the measurements provided by manufacturers
- $X = \text{leakage reactance}$  (combined)
- $X = \text{short-circuit reactance} = \text{reactance seen from port 1 when port 2 is short-circuited}$  (considering that  $X_m$  is very large compared to  $X$ )

# The three-phase transformer
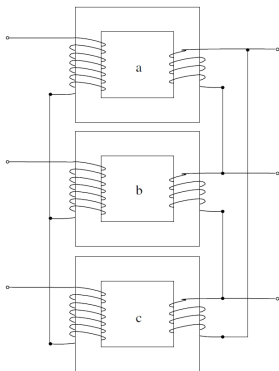
## First type

Three separate single-phase transformers. No magnetic coupling between phases.




Appropriate for transformers of large nominal power:

- in case of failure of one of the transformers, only that transformer is replaced
- easier to carry.
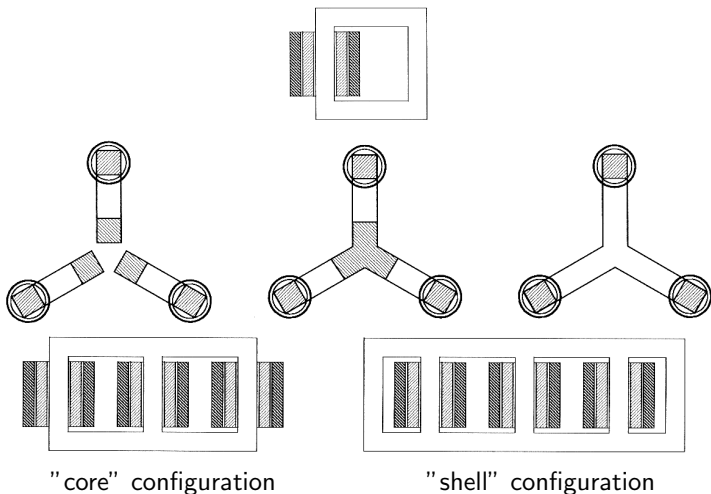
## Second type

The three phases are mounted on a common iron core.



Volume of the common core smaller than three times the volume of a single core.

## Star vs. Delta configuration

Four possible mountings.


- Transformer side connected to extra high voltage network: star configuration preferred since the voltage across each winding is  $\sqrt{3}$  times smaller
- star configuration: possibility to connect the neutral to ground (safety)
- star configuration preferred to place a load tap changer (see later in this chapter)
- transformer side carrying high currents (f.i. the generator side of a step-up transformer): delta configuration preferred since the currents in the branches are  $\sqrt{3}$  times smaller
- delta configuration used to eliminate the harmonics of order 3, 6, 9, etc.

## Single-phase equivalents of three-phase transformers

- transformer with single core: the phases are magnetically coupled  
→ perform a per-phase analysis (see Chapter 2)
- for simplicity, we consider a transformer with three separate cores
- we focus on the impact of the star vs. delta configuration.

### 1. Star-star configuration


Yy0

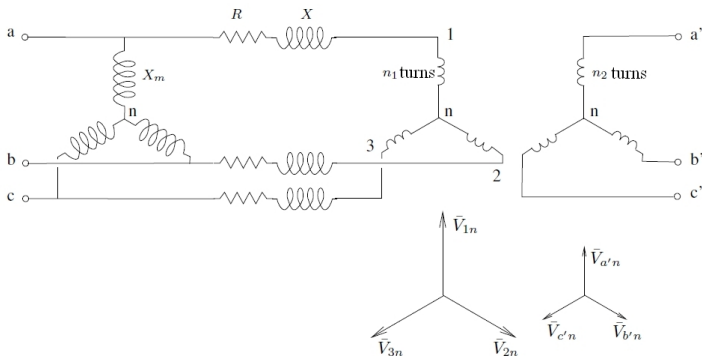


Per-phase equivalent circuit = equivalent circuit of one phase.

## 2. Delta-delta configuration

Dd0


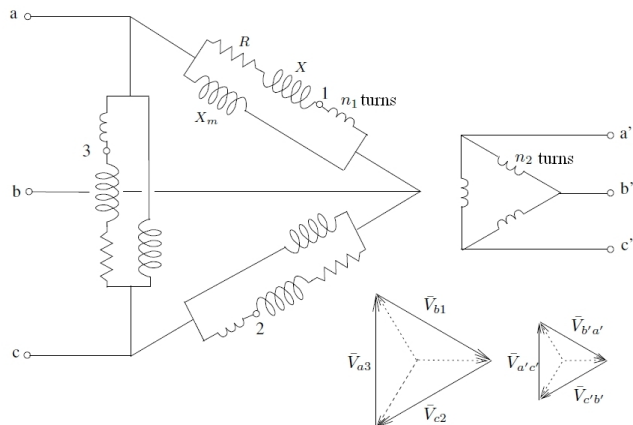


Equivalent circuit:

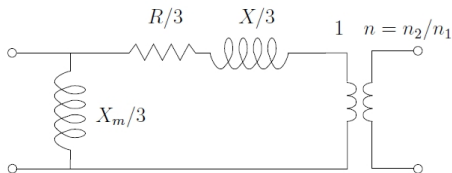

3. Star-delta configuration


Yd11 / Dy1

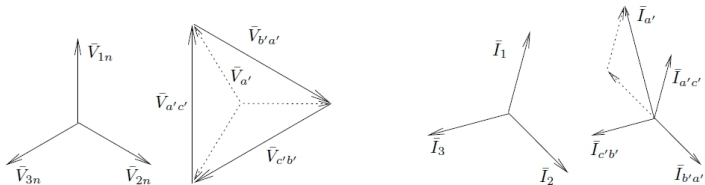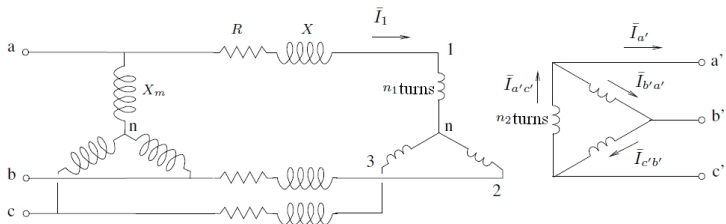

$$\bar{V}_{a'} = \frac{1}{\sqrt{3}} e^{j\pi/6} \bar{V}_{a'c'} = \frac{n_2}{\sqrt{3}n_1} e^{j\pi/6} \bar{V}_{1n} = \bar{n} \bar{V}_{1n} \quad \text{où} \quad \bar{n} = \frac{n_2}{\sqrt{3} n_1} e^{j\pi/6}$$

$$\bar{I}_{a'} = \bar{I}_{a'c'} - \bar{I}_{b'a'} = \sqrt{3} e^{j\pi/6} \bar{I}_{a'c'} = \frac{\sqrt{3} n_1}{n_2} \frac{1}{e^{-j\pi/6}} \bar{I}_1 = \frac{1}{\bar{n}^*} \bar{I}_1$$

Equivalent circuit:

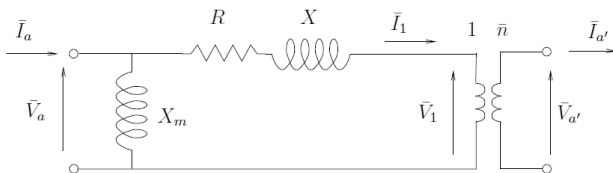

Ideal transformer with complex ratio  $\bar{n}$  :

- is characterized by :  $\bar{V}_{a'} = \bar{n}\bar{V}_1$        $\bar{I}_{a'} = \bar{I}_1/\bar{n}^*$
- reduces to the standard ideal transformer if  $\bar{n}$  is real
- transfers complex power without losses:  $\bar{V}_{a'} \bar{I}_{a'}^* = \bar{n} \bar{V}_1 \frac{1}{\bar{n}} \bar{I}_1^* = \bar{V}_1 \bar{I}_1^*$

The above two-port is *non reciprocal*:  $\begin{bmatrix} \bar{I}_a \end{bmatrix}_{\bar{V}_a=0, \bar{V}_{a'}=1} \neq - \begin{bmatrix} \bar{I}_{a'} \end{bmatrix}_{\bar{V}_a=1, \bar{V}_{a'}=0}$



#### 4. Delta-star configuration

Dy1 / Yd11

Derivation similar to that of the Star-delta configuration,

leading to a single-phase equivalent circuit with:

- the complex transformer ratio:  $\bar{n} = \frac{\sqrt{3} n_2}{n_1} e^{-j\pi/6}$
- a series resistance  $R/3$
- a series reactance  $X/3$
- a shunt reactance  $X_m/3$ .

## Designation of a transformer

Standardized abbreviation of I.E.C. (International Electrotechnical Commission)

Also referred to as *vector group of a transformer*


3 symbols:

- an uppercase letter for the high-voltage side: **Y** for a star connection or **D** for a delta
- a lowercase letter for the low-voltage side: **y** for a star connection or **d** for a delta
- an integer  $p \in \{0, 1, \dots, 11\}$ :
  - an indication of the phase displacement between the primary and secondary voltages of the same phase, the transformer being assumed ideal
  - the phasor of the high voltage being on the number 12 of a clock,  $p$  is the number pointed by the phasor of the low voltage

and for the star configuration:

**n** after **y** or **Y** to indicate that the neutral is grounded.

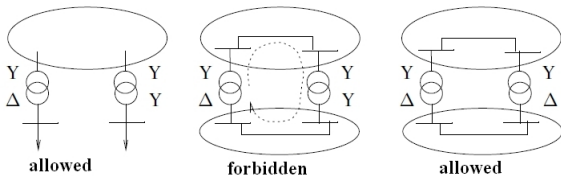
## Caution as regards using transformers with different phase displacements



When a given sub-network is fed by two (or more) transformers operating “in parallel” (i.e. located in at least one loop), the latter must have the same phase displacement  $p$ .

Otherwise, the different phase displacements would cause unacceptable power flows.

## Simplification of computations

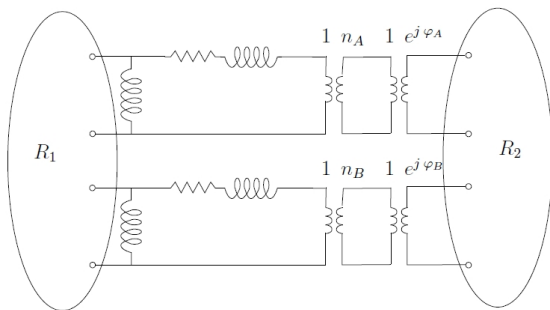

Two transformers with the same phase displacement:  $\varphi_A = \varphi_B = \varphi$

The ideal transformers with complex ratio  $e^{j\varphi}$  can be removed without changing:

- the magnitudes of the branch currents and bus voltages
- the complex powers flowing in the branches.

The phase displacements in the transformer models are ignored when computing the steady-state balanced operation of power systems.

# Nominal values, per unit system and orders of magnitudes

## Nominal values

- Nominal primary voltage  $U_{1N}$  and nominal secondary voltage  $U_{2N}$ : voltages for which the transformer has been designed (in particular its insulation).  
The real voltages may deviate from these values by a few %.
- Nominal primary current  $I_{1N}$  and nominal secondary current  $I_{2N}$ : currents for which the transformer has been designed (in particular the cross-sections of the conductors).  
Maximum currents that can be accepted without limit in time.
- nominal apparent power  $S_N$ :

$$S_N = \sqrt{3}U_{1N}I_{1N} = \sqrt{3}U_{2N}I_{2N}$$

## Conversion of parameters in per unit values

- choose the (three-phase) base power  $S_B = S_N$
- on primary side, choose the (phase-to-neutral) base voltage  $V_{1B} = U_{1B}/\sqrt{3}$
- on secondary side, choose the (phase-to-neutral) base voltage  $V_{2B} = U_{2B}/\sqrt{3}$
- the impedances of the equivalent circuit, which are located on the primary side, are divided by  $Z_{1B} = 3V_{1B}^2/S_B = U_{1B}^2/S_B$
- the value of the transformer ratio  $n = n_2/n_1$  in per unit is obtained as follows:

$$v_2 = \frac{n_2}{n_1} v_1 \quad \Leftrightarrow \quad v_{2pu} = \frac{v_2}{V_{2B}} = \frac{n_2}{n_1} \frac{v_1}{V_{2B}} = \frac{n_2}{n_1} \frac{V_{1B}}{V_{2B}} \frac{v_1}{V_{1B}} = \frac{n_2}{n_1} \frac{V_{1B}}{V_{2B}} v_{1pu}$$

$$\Rightarrow \quad n_{pu} = \frac{n_2}{n_1} \frac{V_{1B}}{V_{2B}}$$

If  $V_{2B}/V_{1B} = n_2/n_1$ :  $n_{pu} = 1$  : the ideal transformer disappears from the equivalent circuit !

In practice,  $V_{2B}/V_{1B} \simeq n_2/n_1$  : the ideal transformer remains in the equivalent circuit but with a ratio  $n_{pu} \simeq 1$ .

## Orders of magnitude

resistance $R$	$< 0.005$ pu
leakage reactance <sup>1</sup> $\omega L$	range: 0.06 – 0.20 pu
magnetizing reactance $\omega L_m$	range: 20 – 50 pu
transformer ratio $n = n_2/n_1$	range: 0.85 – 1.15 pu

values on the  $(S_B, V_{1B}, V_{2B})$  base of the transformer !!

Network computation in another base: convert the parameters to that base (see formula in the chapter on per unit system)


---

<sup>1</sup>or short-circuit reactance

# Autotransformers

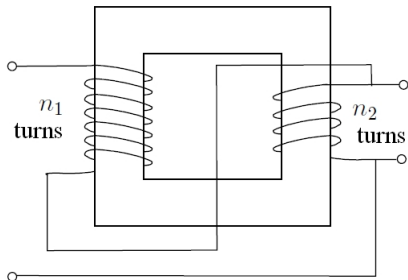
## Single-phase autotransformer

Transformer whose primary and secondary sides are connected in such a way that they have a winding in common:





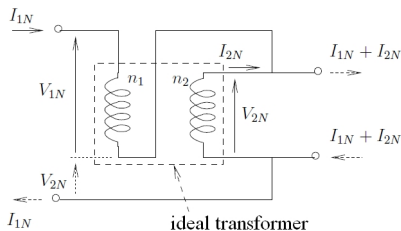Let us assume that the inner transformer operates with its voltages and currents at their nominal values (all losses neglected, transformer assumed ideal).



$$\begin{aligned}
 I_{1N}^{auto} &= I_{1N} & V_{2N}^{auto} &= V_{2N} \\
 V_{1N}^{auto} &= V_{1N} + V_{2N} = \left(1 + \frac{n_2}{n_1}\right) V_{1N} \\
 I_{2N}^{auto} &= I_{1N} + I_{2N} = \left(\frac{n_2}{n_1} + 1\right) I_{2N}
 \end{aligned}$$

Ratio of the autotransformer ?

$$n^{auto} = \frac{V_{2N}^{auto}}{V_{1N}^{auto}} = \frac{V_{2N}}{V_{1N} + V_{2N}} = \frac{\frac{n_2}{n_1}}{1 + \frac{n_2}{n_1}}$$

For the chosen primary and secondary, the transformer is of the step-down type.

Nominal apparent power of the autotransformer ?

$$S_N^{auto} = V_{1N}^{auto} I_{1N}^{auto} = \left(1 + \frac{n_2}{n_1}\right) V_{1N} I_{1N} = \left(1 + \frac{n_2}{n_1}\right) S_N$$


- The autotransformer allows for a power transfer higher than  $S_N$ .  
 $\Rightarrow$  reduced investment costs and reduced losses !
- True for any  $n_1, n_2$  values but for a higher “amplification”:  $n_2 \gg n_1$
- However, if  $n_2 \gg n_1$ , the autotransformer ratio  $n^{auto} \rightarrow 1$ .  
 Hence, the device cannot connect two very different voltage levels
- Autotransformers used to transfer high powers between two networks with relatively close nominal voltages
  - Belgium : 550 MVA autotransformers between 400 and 150 kV
  - France: autotransformers between 400 and 225 kV.
- drawback: metallic connection between primary and secondary  $\Rightarrow$  voltage disturbances propagate more easily.

### Three-phase autotransformer

Assembly of three single-phase autotransformers.

# Adjustment of the turn ratio

## Principle

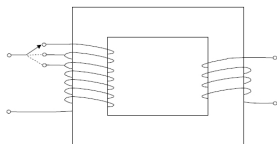

- Objective: adjust voltage at a busbar (usually one of the transformer ends)
- adjustment in steps: between 15 and 25 *tap positions*
- to modify the number of turns in service:
  - transformer taken out of service
  - transformer kept in service: the *on-load (or under-load or load) tap changer* modifies the windings without interrupting the current (avoid electric arcs!)
- load tap changers can be controlled
  - manually: remotely by operator supervising the network from a control center
  - automatically: local feedback system (see chapter on voltage control)
- placement of tap changer:
  - usually on the high-voltage side: current smaller, more turns in winding
  - three-phase transformer: near neutral in Y configuration (lower voltages).

## Accounting the tap position changes in equivalent circuit

In principle, one set of  $(R, \omega L, \omega L_{m1}, n)$  values for **each** tap position.

In practice,  $\omega L$  and  $n$  are the most affected, while  $R \ll$  and  $\omega L_{m1} \gg$ .

Possible simplification: let us assume that:


- the turns are adjusted on side 2 in equivalent circuit
- the leakage inductance  $L_{\ell 2}$  vary with the number of turns  $n_2$  according to:

$$L_{\ell 2} = L_{\ell 2}^o \left( \frac{n_2}{n_2^o} \right)^2$$


- and similarly for the resistance  $R_2$ :

$$R_2 = R_2^o \left( \frac{n_2}{n_2^o} \right)^2$$

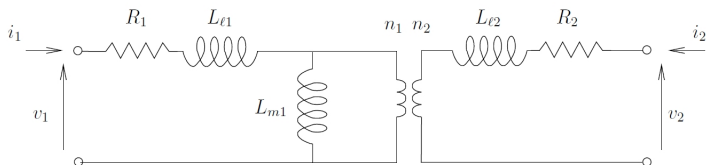This is arguable, but  $R_2$  is small. . .



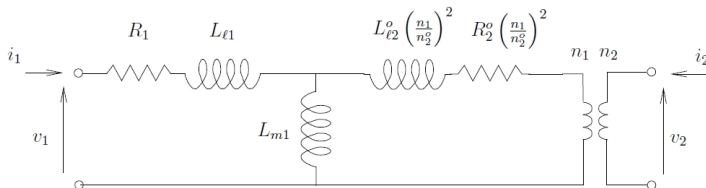After passing  $R_2$  and  $L_{\ell 2}$  on the other side of the ideal transformer:



When the tap position (and, hence, the number of turns  $n_2$ ) changes:


- impedances located on the non-adjusted side remain constant
- only the transformer ratio  $n_2/n_1$  changes.

# Three-winding transformers

Shortcut for “transformers with three windings per phase”.
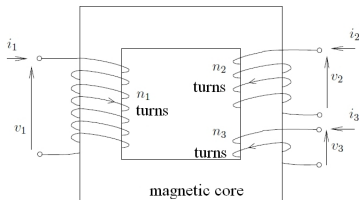
## Principle

Single-phase transformer with 3 windings (= 1 phase of a 3-phase transformer) :




- Power transfer between three voltage levels
- share of power flows between the windings depends on what is connected to the transformer
- nominal apparent powers of the three windings usually different.

## Other uses

- in switching stations, power supplied to auxiliaries by the third winding
- connection of a shunt inductance or capacitor for compensation purposes
- improvement of operation in unbalanced condition
- improvement of power quality in the presence of harmonics.

## Equivalent circuit

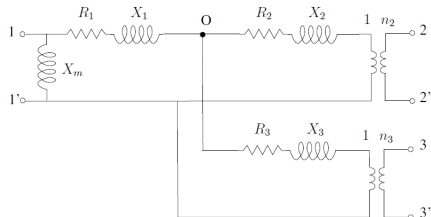

$R_1 + R_2 + j(X_1 + X_2)$  : impedance seen from 1 with 2 short-circuited and 3 opened

$R_1 + R_3 + j(X_1 + X_3)$  : impedance seen from 1 with 3 short-circuited and 2 opened

Some reactances of this equivalent circuit can be negative  
(for instance if the windings have very different nominal apparent powers).

# Phase shifting transformer

Also called simply *phase shifter*.


Transformer aimed at shifting the secondary voltage phasor with respect to the primary voltage phasor, in order to adjust active power flows in the network.

Two main configurations:

- transformer connecting two networks with different nominal voltages (as usual) to which a device is added to adjust the phase angle
- dedicated device, with the *same* primary and secondary nominal voltages, aimed at adjusting the phase angle.




## First scheme

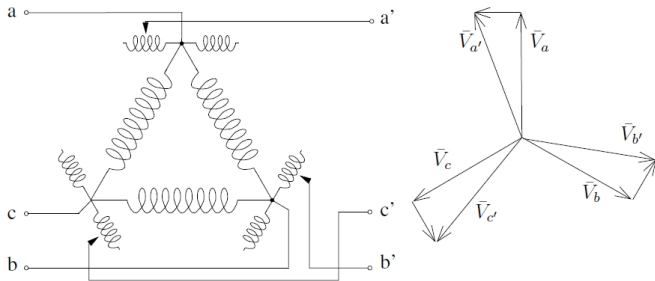

- adjustment *in quadrature*
- some variation of the voltage magnitude with the phase angle
- there exist more elaborate schemes where the voltage magnitude is kept constant while the phase angle is adjusted
- drawback of this scheme: the whole line current passes through the tap changer (unavoidable electric arcs).

## Second scheme

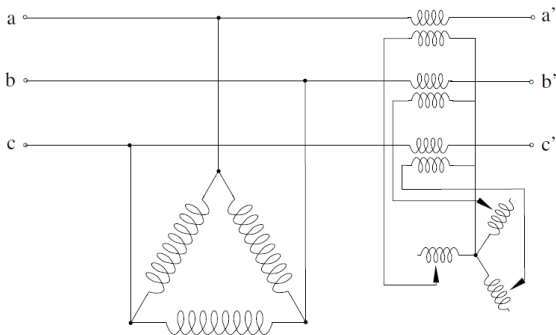

- *excitation* shunt transformer + *series* transformer
- nominal voltage of series transformer = fraction of nominal phase-to-neutral voltage  $V_N \Rightarrow$  nominal apparent power = fraction of  $3V_N I_{max}$
- compared to previous scheme: lower current in the tap changer.

## Example: phase shifting transformers on the borders of Belgium



380/380 kV : in series with:

- ① line Zandvliet (B) - Borssele (NL) and Zandvliet (B) - Geertruidenberg (NL)
  - ② line Meerhout (B) - Maasbracht (NL)
  - ③ line Gramme (B) - Maasbracht (NL)
- nominal power  $3V_N I_{max} = 1400$  MVA
  - phase shift adjustment: 35 positions,  $+17/-17 \times 1.5^\circ$  (at no load)

220/150 kV : in series with the Chooz (F) - Monceau (B) line

- nominal power: 400 MVA
- in-phase adjustment : 21 positions,  $+10/-10 \times 1.5 \%$
- quadrature adjustment: 21 positions,  $+10/-10 \times 1.2^\circ$